
 


TinyMIPS CPU


ECE 4150 Final Project

Nathan Pen and Jaret Williams

 



 Created Tiny MIPS CPU in Verilog
and used Synopsis and Cadence
tools to make one physical chip



Combined all ASIC Design flow
steps learned in class and lab into
one cumulative project

Introduction

Previous Presentation


All Verilog modules of different components done and simulated using a testbench

Connected all components in overall MIPS CPU Verilog module


Initial synthesis of MIPS CPU

What we Have done Since

- Tested functionality of MIPS CPU memory file and Fibonacci instructions in overall test bench
- Inserted Scan Cells into CPU design and synthesized schematic with Scan Cell DFF's
- Performed ATPG test on CPU with Scan Cells inserted and received data for possible Stuck at faults and test patterns
- Completed place and route of synthesized scan cell in Cadence Innovus
- Were able to insert CPU layout and auto route all ports to a pad frame using Cadence

 


ROTATION - HOW TO CODE

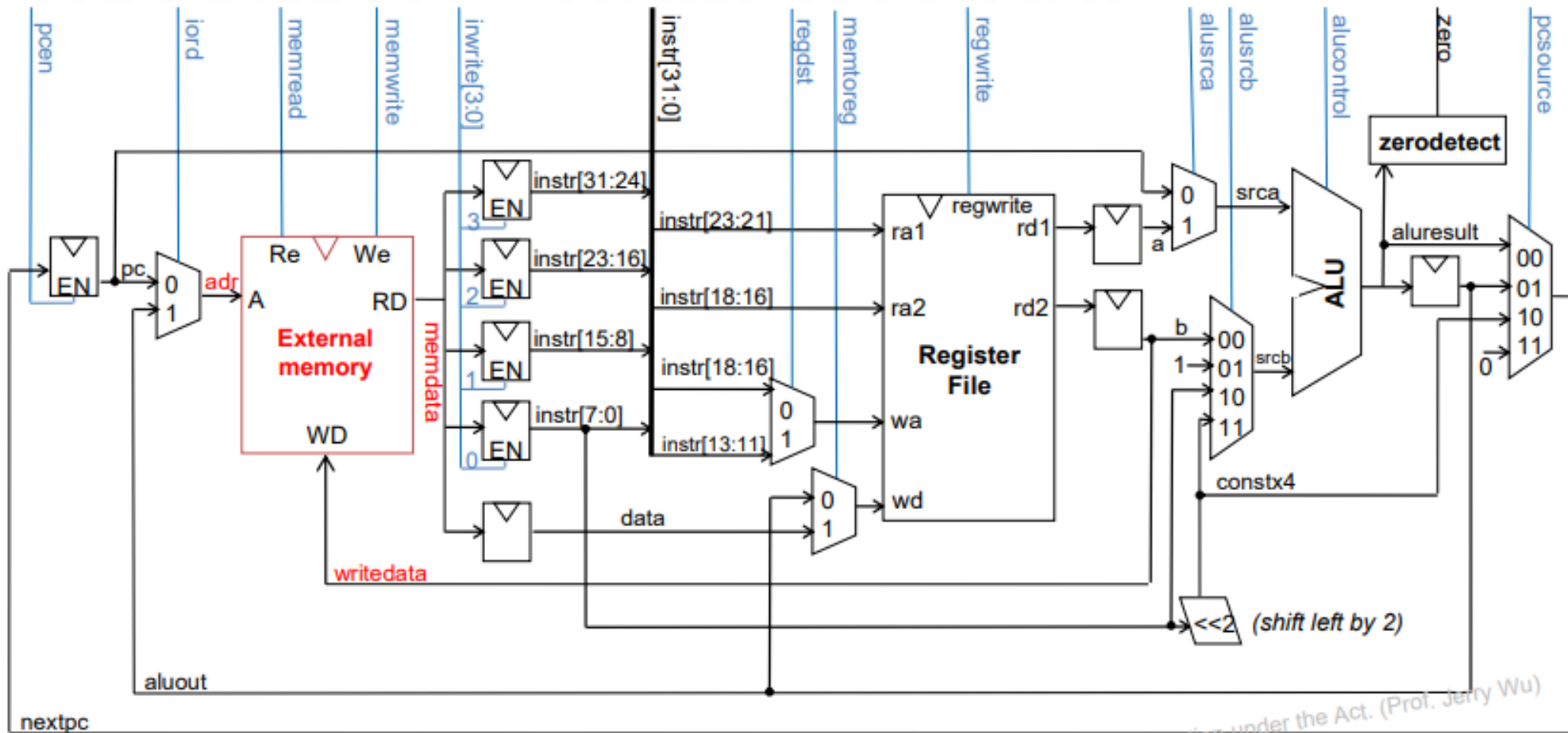

- Everything EXCEPT: **externalMemory** is in the datapath verilog module

R-TYPE INSTRUCTION – RETURN TO STATE 0

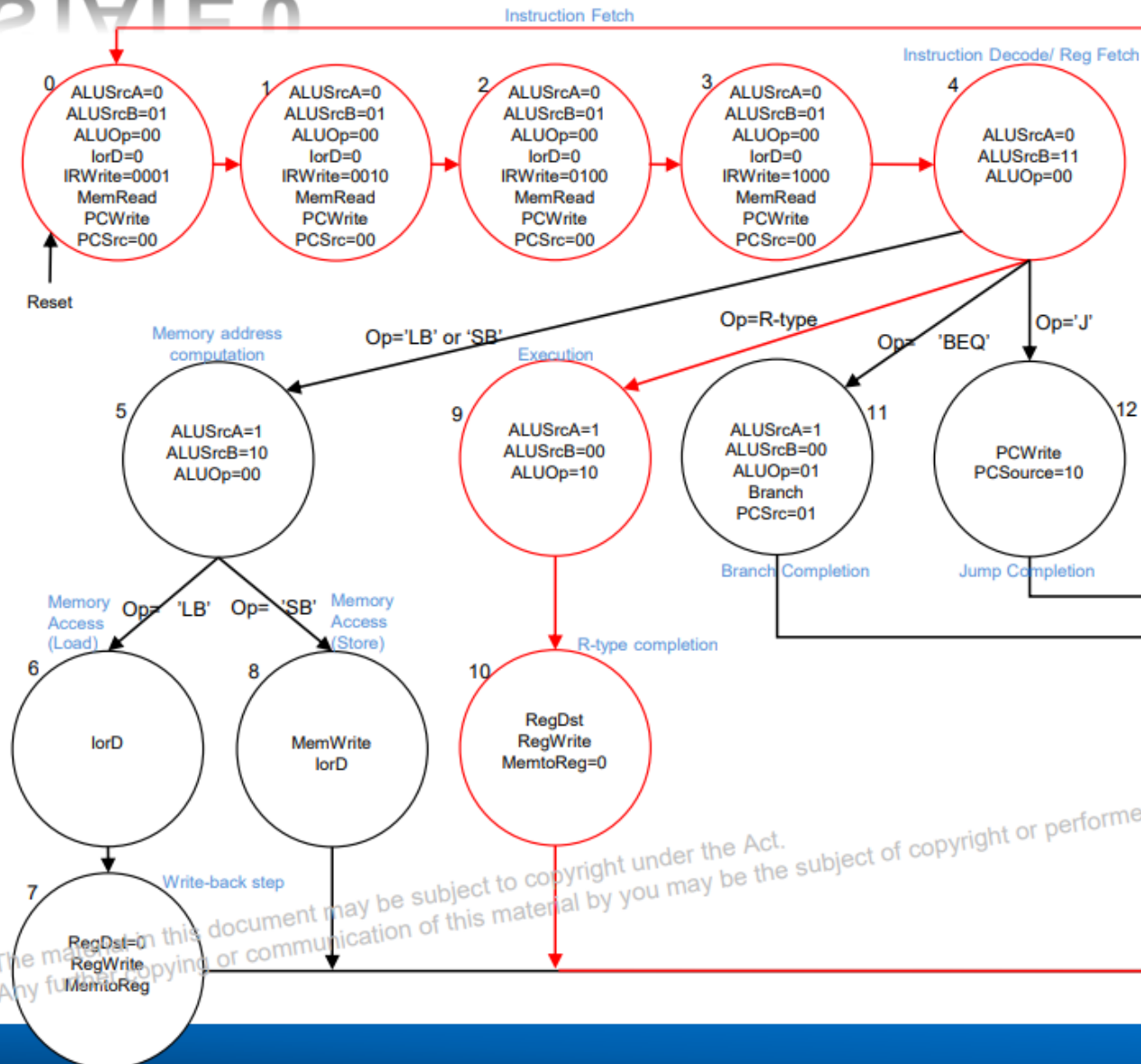

From State 10 back to State 0

- + R-type inst. Is complete
- + Answer is stored in destination register in register file

FSM returns to state 0


- PC has next instruction's address loaded into it.
- That occurred in state 3 to state 4 transition

Dr. Jerry Wu


Full CPU and Memory Verilog Test Bench

```
// top level testing
module top_tb #(parameter WIDTH = 8, REGBITS = 3)();
    parameter FINISHTIME = 20000;
    parameter CLKPERIOD = 20;
    parameter const_gnd = 1'b0;
    reg clk = 0;
    reg reset = 1;
    // testing mips memory module
    mips_mem2 #(WIDTH,REGBITS) dut(.clk(clk), .reset(reset), .const_gnd(const_gnd));
    // initialize
    initial
        begin
            reset <= 1;
            #(4*CLKPERIOD) reset <= 0;
            #FINISHTIME
            $display("Finishing Simulation due to simulation constraint.");
            $finish;
        end
    // clock gen
    always #CLKPERIOD clk <= ~clk;
    // test Fibonacci Simulation
    always@(negedge clk)
        begin
            if(dut.memwrite)
                if(dut.adr == 8'hFF & dut.writedata == 8'h00)
                    begin
                        $display("Fibonacci Simulation was successful!!!");
                        #(4*CLKPERIOD)
                        $display("Ending Simulation.");
                        $finish;
                    end
                else
                    begin
                        $display("Fibonacci Simulation has failed...");
                        $display("Data at address FF should be 00");
                        #(4*CLKPERIOD)
                        $display("Ending Simulation.");
                        $finish;
                    end
            end
        end
    initial
        begin
            $shm_open("top_tb.db");
            $shm_probe(top_tb,"AS");
        end
endmodule
```



Full CPU and Memory Verilog Test Bench

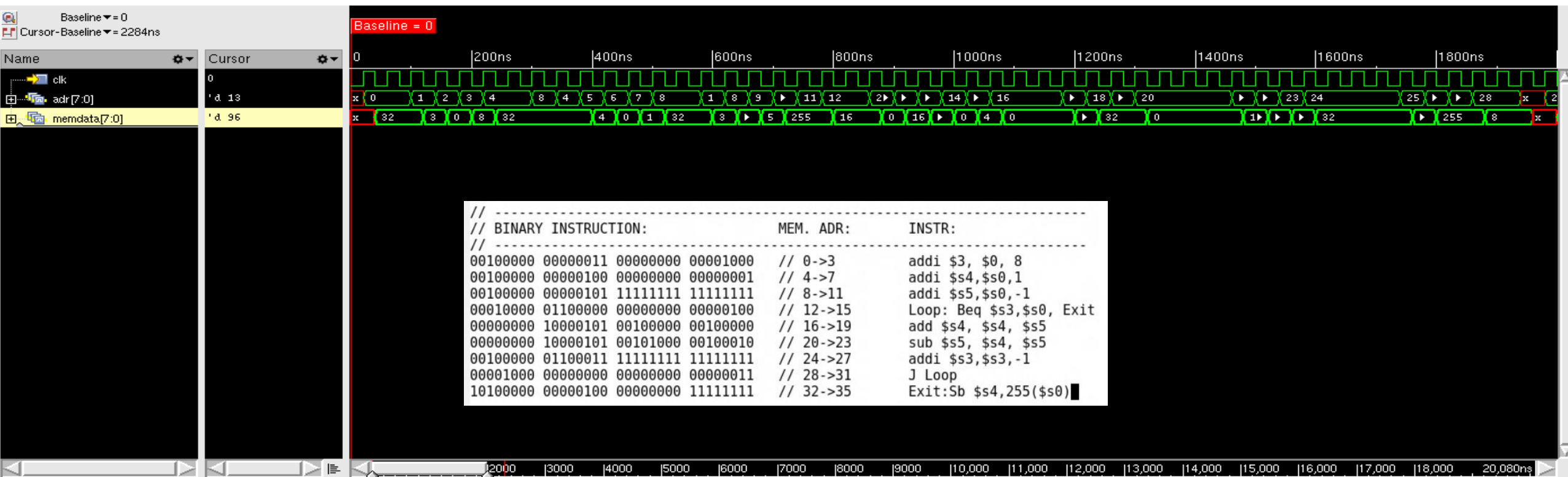

CPU Synthesis

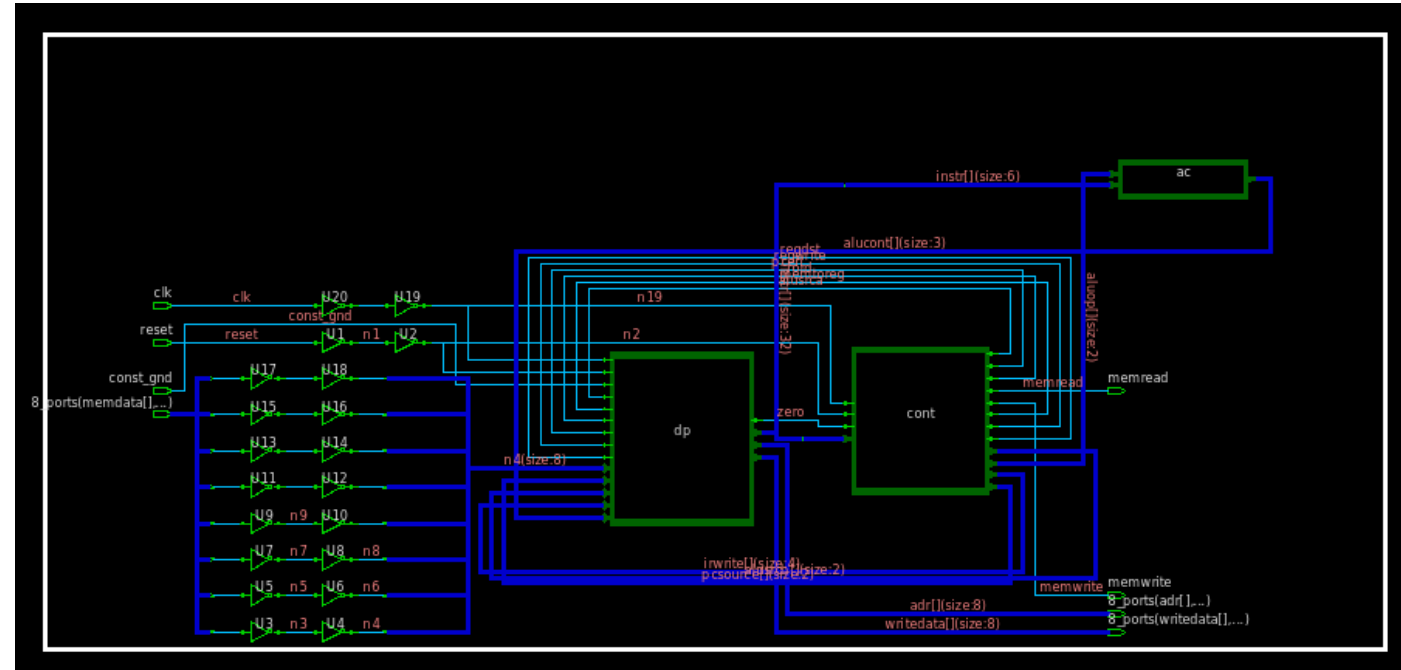


CPU With Scan Cell Synthesis

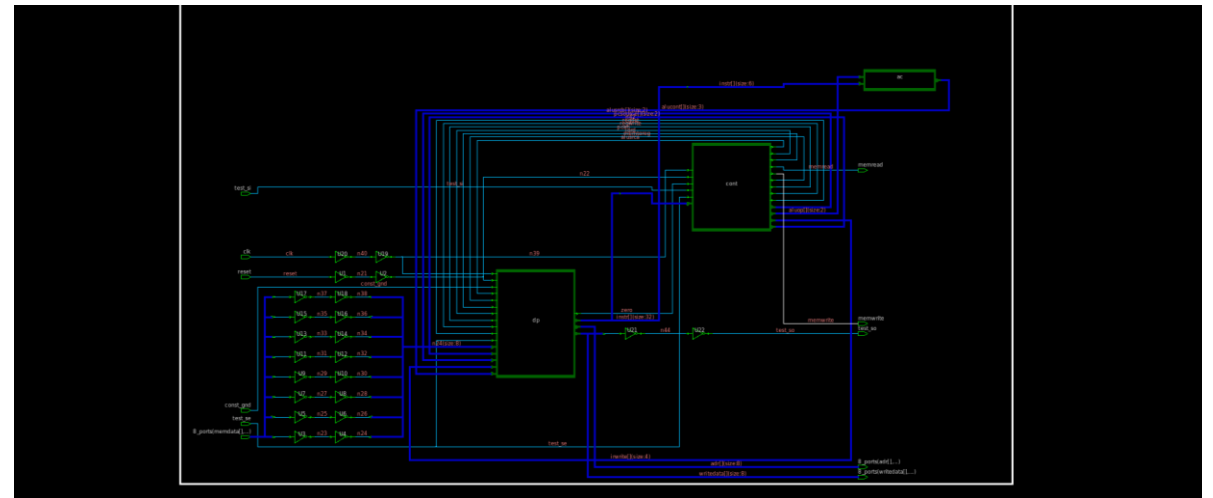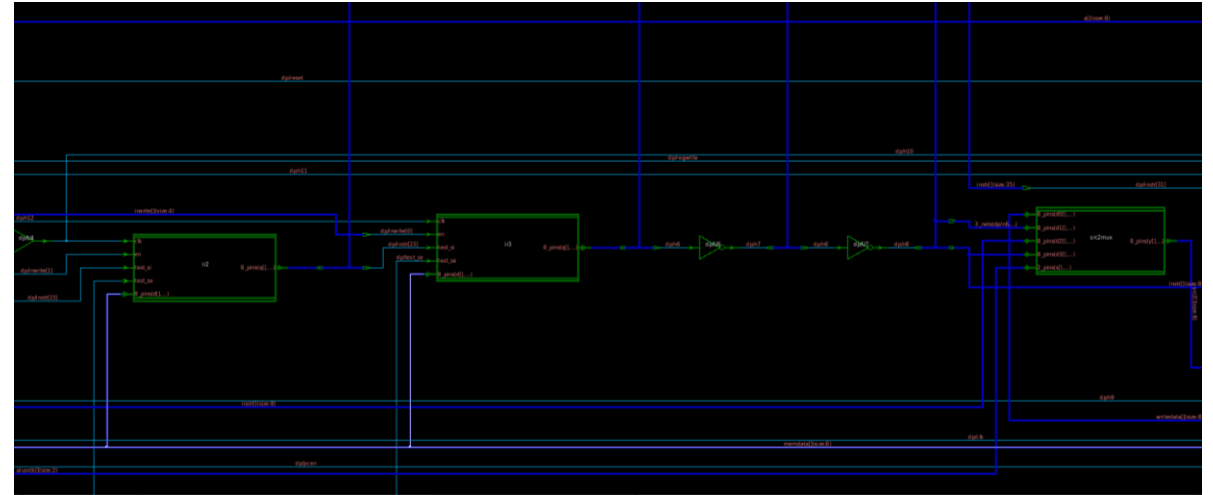


ATPG Test Results

fault class	code	#faults
Detected	DT	5971
Possibly detected	PT	0
Undetectable	UD	39
ATPG untestable	AU	0
Not detected	ND	0
total faults		6010
test coverage		100.00%

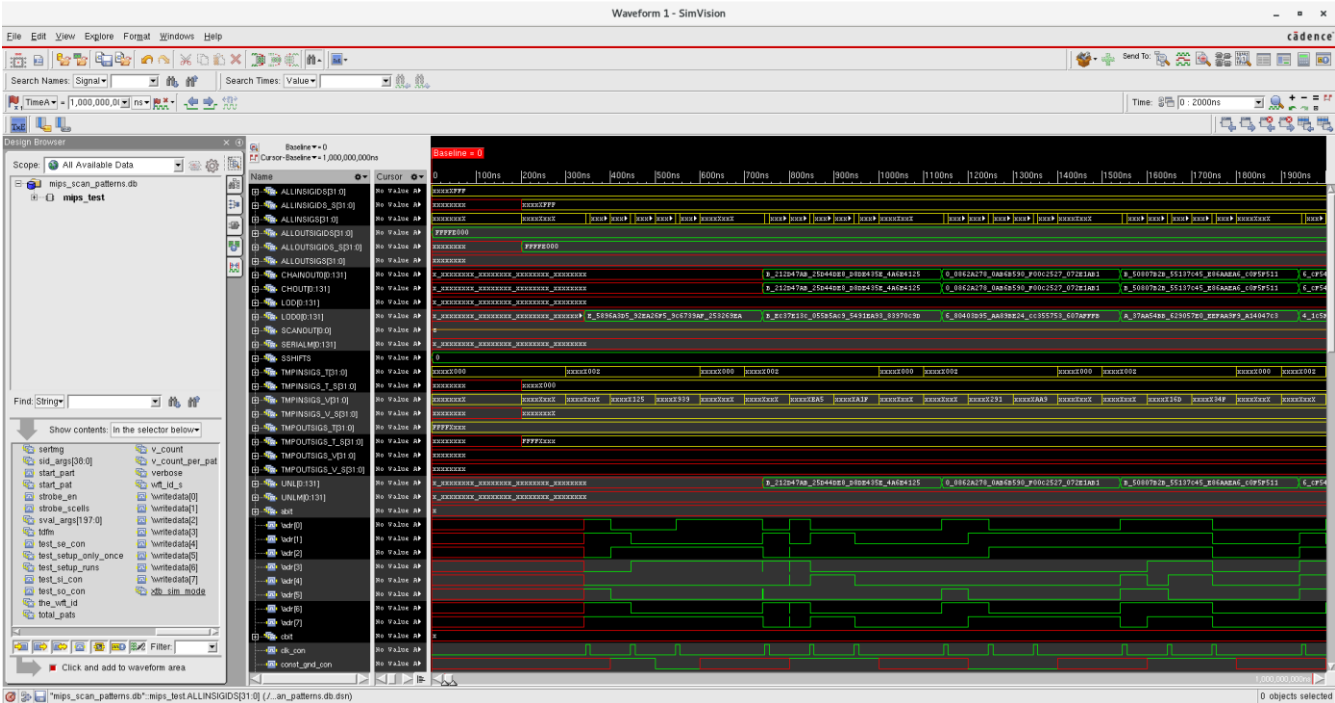
Information: The test coverage above may be inferior than the real test coverage with customized protocol and test simulation library.




Place and Route of CPU

 


CPU Circuit in Cadence

 


Pad frame Schematic

 


CPU in Pad Frame

 

Auto Routing Video

 

CPU Routed in Pad Frame

 

Challenges

- Following overall test bench simulation to ensure proper operation of CPU with memory file
 - Found error in Datapath file
- Had to redo Synthesis of design with Scan Cell because were missing .sdc file
- Had to redo Place and Route with updated default.view file
- Had to ensure all padframe files were in the same libraries linked to the same tech libraries to complete auto routing



Final Steps



Submit GDS File with final report



Get layout Fabricated if possible



Do testing on physical chip

Questions?

